

From the circuit diagram, the BTNx is active High or active Low? Please provide your analysis.

Since the button gives 3.3v when pressed, and 0v when idle, it's **Active High**

What is a bounce? How do you programmatically debounce the input? Please provide your analysis.

Bounce means when the physical input oscillates cause digital input read value switched between 0 and 1 rapidly for a period of time.

To debounce divide a clock into slower cycle holding time for input to get steady.

Please show your method for implementing a single pulser. (e.g. draw a state diagram, or verilogHDL code)

```
module singlePulser(  
    output reg d,  
    input clk, pushed  
);  
reg ps;  
  
initial ps=0;  
  
always @(posedge clk)  
begin  
    d = 0;  
    if (pushed == ~ps) begin  
        if(ps == 1)  
            ps=0;  
        else if (pushed == 1) begin  
            d = 1;  
            ps = 1;  
        end  
    end  
end  
endmodule
```